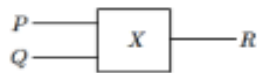


Assignment #3SIMPLIFY THE BOOLEAN FUNCTION USING BOOLEAN ALGEBRA

1.  $AB + A(B + C) + B(B + C)$
2.  $AB' + A(B + C)' + B(B + C)'$
3.  $[AB'(C + BD) + A'B']C$
4.  $A'BC + AB'C' + A'B'C' + AB'C + ABC$
5.  $((A + B)' + C)'$
6.  $(a+b'+c+d')+(b+c')$
7.  $x'y'z + yz + xz$
8.  $(A + B' + C')(A + B' + C)(A + B + C')$
9.  $XY + X(Y' + Z)' + Y(Y + Z)$
10.  $(XY(Y'Z + XZ))'$
11. Express the Boolean function  $F = A + B'C$  in a sum of minterms (SOP).
12. Express  $F = xy + x'z$  in a product of maxterms form.
13. How many different Boolean functions of  $n$  variables are there?
14. Find out the dual of the given Boolean function  $AB'C + BC' + AC'$ .
15. How many number of self dual functions of  $n$  variables?
16. Simplify the following Boolean expression using Karnaugh map:  $F(x,y,z) = \Sigma(3,4,6,7)$
17. Simplify the following Boolean expression using Karnaugh map:  $F(x,y,z) = \Sigma(0,1,2,4,5,6)$
18. Simplify the following Boolean expression using Karnaugh map:  
 $F(w,x,y,z) = \Sigma(0,1,2,4,5,6,8,9,12,13,14)$
19. Simplify the following Boolean expression using Karnaugh map:  
 $F(w,x,y,z) = \Sigma(0,2,3,5,7,8,9,10,11,13,15)$
20. Simplify the following Boolean function in sum of minterm:  
 $F(A, B, C, D) = \Sigma(0, 6, 8, 13, 14)$  d  $(A, B, C, D) = \Sigma(2, 4, 10)$   
where, d stands for don't care condition
21. Simplify the following Boolean expression using Karnaugh map:  
 $F(w,x,y,z) = \Sigma(1,3,7,11,15) + x(0,2,5,8)$
22. What is the logic equation of an EX-NOR gate having A and B as its input?

23. : Logic gates  $X$  and  $Y$  have the truth tables shown below:



$X$		
$P$	$Q$	$R$
0	0	0
1	0	0
0	1	0
1	1	1




$Y$	
$P$	$R$
0	1
1	0

When the output of  $X$  is connected to the input of  $Y$ , the resulting combination is equivalent to a single:

1. NOT gate
2. OR gate
3. NAND gate
4. AND gate

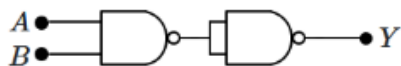24.


Following diagram performs the logic function of:



1. AND gate
2. NAND gate
3. OR gate
4. XOR gate

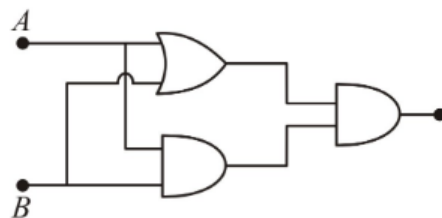25.


The combination of gates shown in the diagram is equivalent to:



1. OR
2. AND
3. NAND
4. NOT

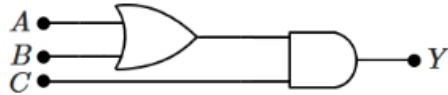26.


To get output  $Y = 1$  for the following circuit, the correct choice for the input is:



1.	$A = 1, B = 0, C = 0$
2.	$A = 1, B = 1, C = 0$
3.	$A = 1, B = 0, C = 1$
4.	$A = 0, B = 1, C = 0$

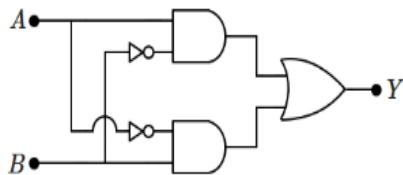27.

For the logic circuit given below, the output  $Y$  for  $A = 0, B = 0$  and  $A = 1, B = 1$  are:



1. 0 and 1
2. 0 and 0
3. 1 and 0
4. 1 and 1

28.

The output of the OR gate is 1:

1.	only if both inputs are zero.
2.	if either or both inputs are 1.
3.	only if both inputs are 1.
4.	if any of the inputs is zero.